

071305T4EOP

ELECTRICAL OPERATION (POWER OPTION)

LEVEL 5 ENG/OS/PO/CC/01/5

APPLY ELECTRICAL

PRINCIPLES July/August 2024

Time: 3 Hours



TVET CURRICULUM DEVELOPMENT, ASSESSMENT AND
CERTIFICATION COUNCIL (TVET CDACC)

WRITTEN ASSESSMENT

TIME 3 HOURS

Answers

SECTION A (40 MARKS)

1. **Ohm's Law:** Ohm's Law states that the current (I) flowing through a conductor between two points is directly proportional to the voltage (V) across the two points and inversely proportional to the resistance (R) of the conductor. Mathematically, it is expressed as: $V = I \times R$ or $I = \frac{V}{R}$
2. **Resistor Voltage (V) vs. Time (S) Characteristic Curve:**
 - The curve typically shows an exponential rise in voltage across the capacitor as it charges over time.
 - (I can't draw here, but you can sketch a graph with time on the x-axis and voltage on the y-axis, showing a curve that starts at zero and asymptotically approaches the supply voltage.)
3. **Electrical Instruments to Measure Current:**
 - **Ammeter:** Used for measuring current in a circuit.
 - **Clamp Meter:** Measures current without needing to disconnect the circuit.
4. **Current Calculation:** $I = \frac{Q}{t} = \frac{240 \text{ C}}{2 \times 60 \text{ s}} = 2 \text{ A}$
5. **SI Units:** SI units stand for **Système International d'Unités**.
6. **Power Dissipated by a Resistor:** $P = I^2 \times R = (2 \text{ A})^2 \times 10 \Omega = 40 \text{ W}$

7. **Energy Consumed by the Resistor:**

$$E = P \times t = (I^2 \times R) \times t = (2 \text{ A})^2 \times 100 \text{ } \Omega \times (10 \times 3600 \text{ s}) = 1440000 \text{ J} = 1440 \text{ kJ}$$
$$E = P \times t = (I^2 \times R) \times t = (2 \text{ A})^2 \times 100 \text{ } \Omega \times (10 \times 3600 \text{ s}) = 1440000 \text{ J} = 1440 \text{ kJ}$$

8. **Major Components of a Solar PV System:**

- Solar Panels (Photovoltaic Modules)
- Inverter
- Charge Controller
- Battery Storage System

9. **Current Calculation for Each Resistor:**

- a) $I = 50 \text{ V} / 22 \text{ } \Omega \approx 2.27 \text{ A}$ $I = 22 \text{ } \Omega / 50 \text{ V} \approx 0.44 \text{ A}$
- b) $I = 50 \text{ V} / 820 \text{ } \Omega \approx 0.061 \text{ A}$ $I = 820 \text{ } \Omega / 50 \text{ V} \approx 0.016 \text{ A}$
- c) $I = 50 \text{ V} / 330,000 \text{ } \Omega \approx 0.000152 \text{ A}$ $I = 330,000 \text{ } \Omega / 50 \text{ V} \approx 6600 \text{ A}$

10. **Ways to Interconnect Phases:**

- **Star Connection:** Reduces the number of conductors by using a common neutral.
- **Delta Connection:** Allows for three-phase loads to be connected with fewer conductors.

11. **Phase and Line Currents and Voltages in Star Connection:**

- $V_L = 3 \times V_P$ $V_L = 3 \times V_P$
- $I_L = I_P$ $I_L = I_P$

12. **Methods to Measure Power in a Three-Phase System:**

- **Wattmeter Method**
- **Two-Wattmeter Method**
- **Three-Wattmeter Method**

13. **Definitions Related to Fuses:**

- a) **Current Rating of a Fuse:** The maximum current that a fuse can carry without blowing.
- b) **Fusing Current:** The current at which the fuse element melts, causing the fuse to blow.

14. **Norton's Theorem:** To determine the current flowing through the $5 \text{ } \Omega$ resistor, you would need the circuit diagram to apply Norton's theorem, which involves finding the equivalent current source and parallel resistance.

SECTION B (60 MARKS)

15. a) i. **Causes of Low Power Factor:**

- Inductive loads (e.g., motors, transformers).

- Capacitive loads (e.g., capacitor banks).

ii. Ways to Improve Power Factor:

- Installing power factor correction capacitors.
- Using synchronous condensers.

b) Calculating Current at Each Power Factor:

- i. $I = \frac{P}{V \times PF} = \frac{1840 \text{ W}}{230 \text{ V} \times 1} \approx 8 \text{ A}$ $AI = V \times PFP = 230 \text{ V} \times 11840 \text{ W} \approx 8 \text{ A}$
- ii. $I = \frac{1840 \text{ W}}{230 \text{ V} \times 0.8} \approx 10 \text{ A}$ $AI = 230 \text{ V} \times 0.81840 \text{ W} \approx 10 \text{ A}$
- iii. $I = \frac{1840 \text{ W}}{230 \text{ V} \times 0.4} \approx 20 \text{ A}$ $AI = 230 \text{ V} \times 0.41840 \text{ W} \approx 20 \text{ A}$

iv. **Justification:** As power factor decreases, the current increases for the same power level, indicating less efficiency.

16. a) i. Reasons for Earthing:

- Safety from electric shock.
- Protection of equipment from lightning.
- Stabilizing voltage levels.

ii. Methods of Achieving Earthing:

- Rod Earthing.
- Plate Earthing.
- Strip Earthing.

iii. Tests Related to Earthing:

- Earth Resistance Test.
- Earth Continuity Test.

iv. Components of Lightning Protection System:

- Air Termination Rods.
- Down Conductors.
- Earth Termination System.

17. a) Diagram of a DC Machine: (You will need to draw a labeled diagram showing stator, rotor, commutator, brushes, etc.)

b) Single-Phase Capacitor Start Motors: (You will need to draw a labeled diagram and explain the role of the capacitor in starting the motor and its phasor representation.)

c) Transformer Losses: i. **Copper Losses:** Losses due to resistance in the winding when current flows (I^2R losses). ii. **Iron Losses:** Losses due to hysteresis and eddy currents in the core.

18. a) **Average Rate of Cooling:**

- Calculate the total heat absorbed by the ice using specific heat and latent heat, then divide by time to find kJ/hr and TR.

b) **Refrigeration Effect and COP:**

- Calculate the refrigeration effect using the latent heat and mass flow rate, then find TR and COP based on energy consumed.